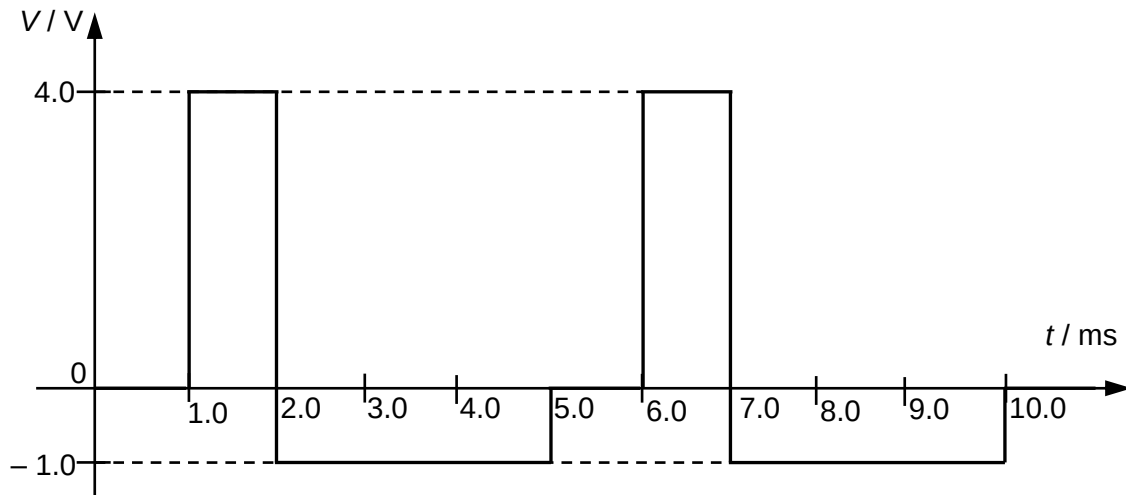


27

The variation with time t of the voltage V of an alternating source applied across a $2.5\ \Omega$ resistor is shown below.



What is the mean power dissipated in the resistor?

[Turn over

	A 0.98 W	B 1.5 W	C 1.9 W	D 2.4 W
	Answer: B To find r.m.s. value of V, we need to square the graph and find the average value of V^2 then find square root. $V_{\text{r.m.s.}} = \sqrt{\frac{(4^2 \times 1) + (1 \times 3)}{5}} = \sqrt{3.8}$ Power dissipated = $V_{\text{r.m.s.}}^2 / R = 3.8 / 2.5 = 1.5 \text{ W}$			