

23 A

The bulb with the largest current flowing through it will be brightest as power = I^2R . Hence bulb P is the brightest.

24 D