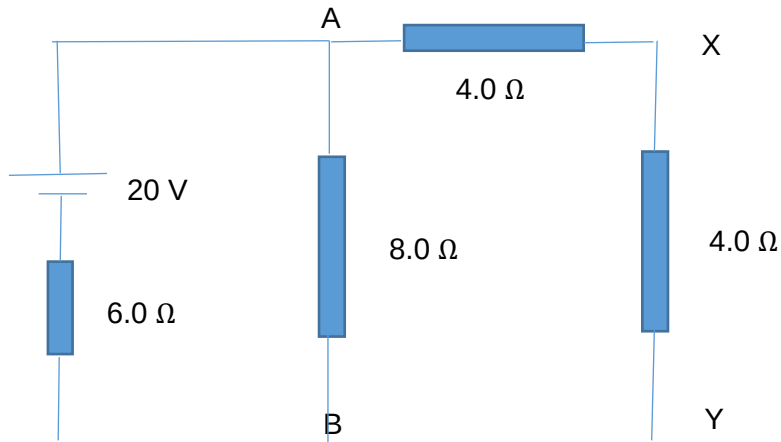


24

Answer: B



Effective resistance between X and Y = $4.0\ \Omega$

Effective resistance between A and B = $\frac{1}{2} (8.0) = 4.0\ \Omega$

By potential divider rule, potential difference between A and B = $20 \times 4.0 / (6.0 + 4.0)$
 $= 8.0\ \text{V}$

Therefore potential difference between X and Y = $\frac{1}{2} (8.0) = 4.0\ \text{V}$

10

25

Answer: A