

Qns	Answer	Marks
5(a)	$R_{diode} = \frac{V}{I} = \frac{0.56}{6.0 \times 10^{-3}} = 93 \, \Omega$	A1
5(b)	$E = V_{diode} + V_{R3}$ $1.2 = 0.56 + (6.0 \times 10^{-3})R_3$ $R_3 = 110 \, \Omega$	C1 A1
5(c)	$I = \frac{E}{R_1 + R_2}$ $= \frac{1.2}{50 + 200}$ $= 4.8 \times 10^{-3} \, A$	C1 A1
5(d)	$I_{total} = 6.0 \times 10^{-3} + 4.8 \times 10^{-3} = 1.1 \times 10^{-2} \, A$ $P = I_{total}E = (1.1 \times 10^{-2})(1.2)$ $P = 1.3 \times 10^{-2} \, W$	C1 A1
5(e)	$\frac{x}{1.0} = \frac{50}{250}$ $x = 0.20 \, m$	C1 A1

