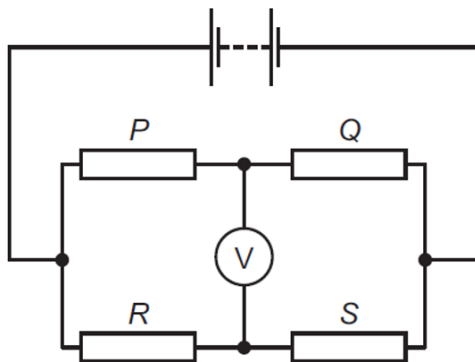


19 The circuit diagram shows four resistors of different resistances P , Q , R and S connected to a battery.

13



The voltmeter reading is zero.

Which equation is must be correct?

- A** $P - Q = R - S$
- B** $P - S = Q - R$
- C** $PQ = RS$
- D** $PS = QR$

Ans: D

Since voltmeter reading is zero, it means no current passes through it.

Current in P = current in Q and current in R = current in S

$$\frac{P}{Q} = \frac{R}{S}$$

$$PS = QR$$