

$$a = 1.90 \text{ m/s}$$

20 B Since current is flowing through the specimen, current must be the same in each section.

$$I_X = I_Y = I_Z$$

Since $I = nevA$, as I , n and e are constant, v is inversely related to A .

$$V_X > V_Z > V_Y$$

21 C p.d. across the $400 \, \Omega$ resistor = p.d. across the $600 \, \Omega$ resistor