

5 (a) $Q = It = 0.150 \times 20 \times 60 = 180 \text{ C}$

(b) $V = IR = 0.150 \times 12 = 1.8 \text{ V}$

(c) Using the potential divider principle,

$$\frac{12}{12 + R_{eff}} \times 6.0 = 1.8$$

$$12 + R_{eff} = 40$$

$$R_{eff} = 28 \Omega$$

Since 33Ω resistor and resistor R are arranged in parallel,

$$\frac{1}{33} + \frac{1}{R} = \frac{1}{28}$$

$$R = 185 \Omega$$

(d) As the temperature of the thermistor increases, the resistance of the thermistor decreases.

The equivalent resistance across the parallel combination of thermistor and 33Ω resistor will decrease and the effective resistance of the circuit will decrease.

The ammeter reading will increase.

6 (a) $\phi = BAN$