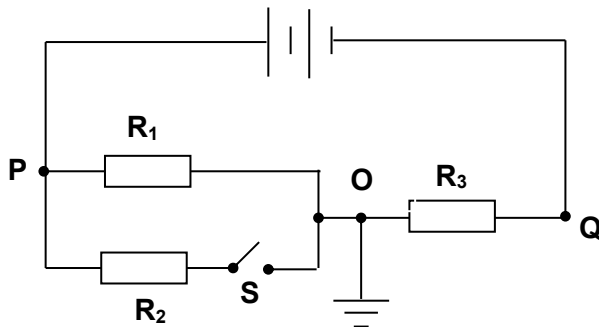


$$y = 3y_1 = 3(9.45 \times 10^{-3}) = 28 \text{ mm}$$

20

D



Let point O be the point of zero potential.

When switch S is closed, resistance between OP will reduce. Using the principle of potential divider, the p.d. between OP also reduces which leads to a lower potential at P (lower positive potential value).

Since p.d between OP reduces, it will lead to a larger p.d. between OQ and a lower potential at Q (lower negative potential value).

21

A

Using $I = Ne/t$