

Hence, the forces acting on the ring will alternate periodically.

25 Ans: B

The output voltage is $240/20 = 12$ V, and output current is $12/5$. Output power is $12 \times 12/5$, which is 0.95 of the input power.

$$\frac{12 \times 12}{5} = 0.95 \times 240 I$$
$$I = 0.126 \text{ A}$$

26 Ans: B