

terminal p.d will increase.

20. Ans: B

Explanation: using potential divider, potential at top left corner will be 6 V while potential at bottom right corner will be 4 V. Thus potential difference as read by voltmeter will be 2 V.

21. Ans: B