

Q23

Note: A diode arranged in series with a resistor will give a half-wave rectified waveform with a

rms current $I_{rms} = \frac{I_0}{2}$.

When the $1000\ \Omega$ resistor is conducting, peak current = $12/1000 = 0.012$ A. Root mean square current is

$$I_1 = \frac{0.012}{2} = 0.0060\text{ A (first half cycle)}$$

When the $2000\ \Omega$ resistor is conducting, peak current = $12/2000 = 0.0060$ A. Root mean square current is

$$I_2 = \frac{0.0060}{2} = 0.0030\text{ A (second half cycle)}$$

Total Average power $\langle P \rangle = I_1^2 R_1 + I_2^2 R_2 = 0.006^2(1000) + 0.003^2(2000) = 0.054\text{ W}$

Ans: B

Q24