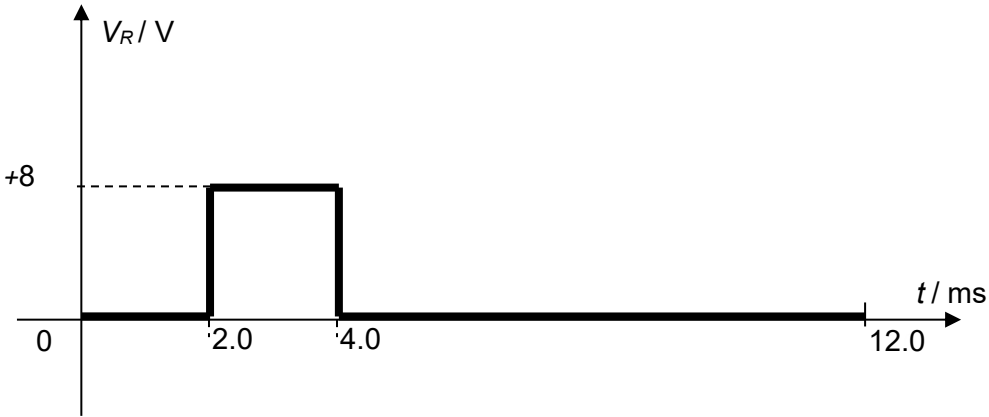


|   |        |                                                                                                                                                                                                                |                                   |
|---|--------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------|
| 5 | a      | <p>By transmitting electrical power in a.c. mode, the <u>transmission voltage can be stepped up.</u></p> <p>This will <u>reduce power loss</u> in the cables due to a <u>smaller transmission current.</u></p> | <p><b>M1</b></p> <p><b>A1</b></p> |
|   | b(i)   | $V_{\text{rms}} = \sqrt{\frac{2(10.0)^2(2.0) + (20.0)^2(2.0) + 2(10.0)^2(2.0) + (20.0)^2(2.0)}{12.0}}$ $= 14 \text{ V}$                                                                                        | <p><b>C1</b></p> <p><b>A1</b></p> |
|   | (ii)1. | 0 V                                                                                                                                                                                                            | <b>A1</b>                         |
|   | (ii)2. | <p>p.d. across resistor <math>R = 20 - 12</math><br/> <math>= 8.0 \text{ V}</math></p>                                                                                                                         | <p><b>C1</b></p> <p><b>A1</b></p> |
|   | (iii)  |  <p>correct shape of graph.<br/> value + 8 V labelled (awarded if graph is correct)</p>                                     | <p><b>M1</b></p> <p><b>A1</b></p> |
|   |        | Total:                                                                                                                                                                                                         | <b>9</b>                          |