
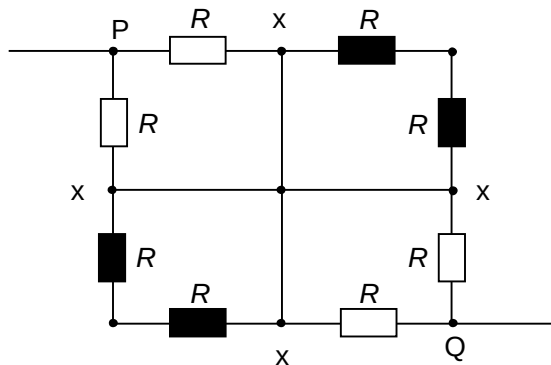


18

Ans: C

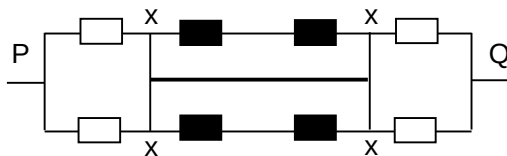

The above circuit can be redrawn as:



No current passes through the resistors in black as all current will pass through the bold wire (zero resistance)

Resistance across PQ = $R/2 + R/2 = R$

19

Ans: D