

	frequency / Hz	
5ai	As V increases, power dissipation increases, which <u>increases</u> the <u>temperature</u> of the filament. The <u>amplitude</u> of vibration of <u>lattice ions/atomic core</u> increases, causing electrons to <u>collide more frequently</u> with the lattice ions/atomic core as they drift along the filament. This <u>reduces</u> the <u>mean drift speed</u> of the electrons. Hence resistance increases.	B1 B1 B1
5aii	Straight line passing through origin and (6.0, 250)	B1
5aiii	$\text{change in resistance} = \frac{6.0}{0.250} - \frac{4.0}{0.205}$ $= 4.5 \, \Omega$	C1 A1
5bi	The effective resistance of the LDR and lamp is less than $10 \, \Omega$ in daylight. Using the potential divider principle, potential difference across the lamp (and LDR) will be less than 6 V (or less than 4 V).	B1 B1

