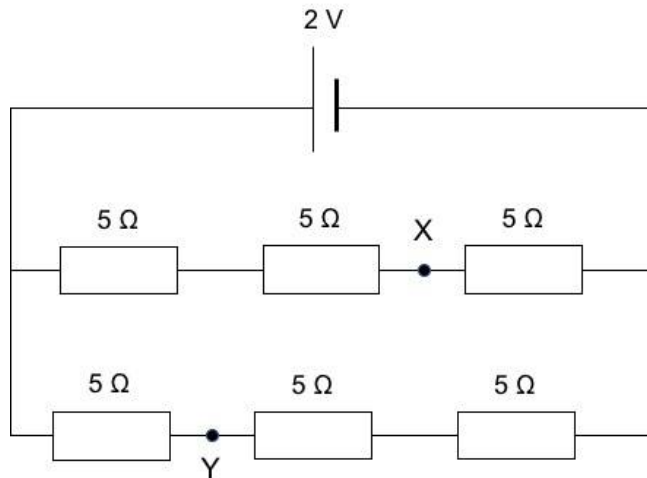


$$= 1.44 \text{ A}$$

22
L2

Solution: **B**

The diagram can be re-drawn as shown:



the resistors are all with the same resistance,
the potential drop across each resistor $= \frac{1}{3} (2) = \frac{2}{3} \text{ V}$

potential at X is $= \frac{2}{3} \text{ V}$.

potential at Y is $2 \times \frac{2}{3} = \frac{4}{3} \text{ V}$.

potential difference between XY is

$$\frac{4}{3} - \frac{2}{3} = \frac{2}{3} \text{ V}$$

23	Solution: C	