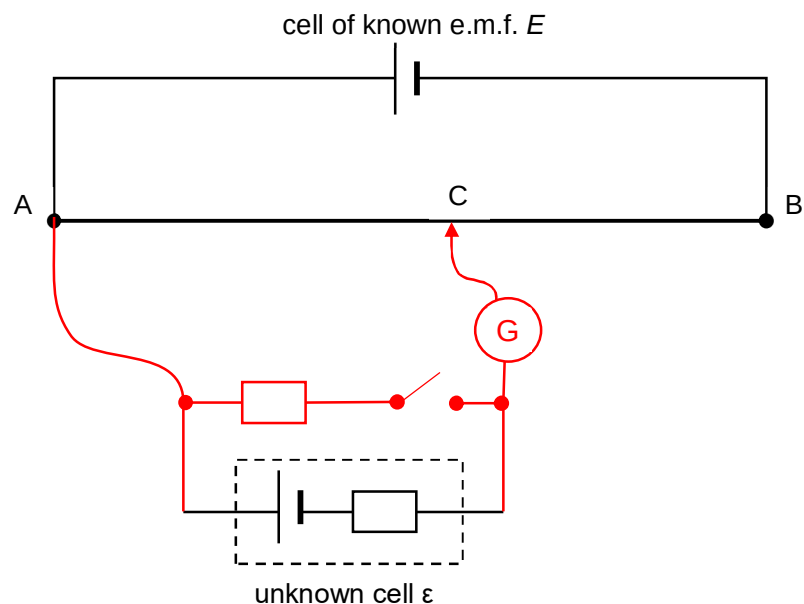


5(a)



- Correct drawing with switch in the correct position.

B1

Turn off the switch. Find balance length when galvanometer shows null reading.

B1

Find ϵ using $\epsilon = V_{AC} = kL_{AC}$ and $V_{AB} = E = kL_{AB}$

Turn on the switch.

Find the new balance length, L_{AC}'

B1

To find r:

Compare $V_{AC}' = kL_{AC}'$ and $V_{AB} = E = kL_{AB}$

$V_{AC}' = kL_{AC}' = (R/R+r) \cdot \epsilon$

Solve r.

Question	Marks
5(b)(i) For single strand: $R = \frac{\rho L}{A}$ $= \frac{(4.9 \times 10^{-7})(1)}{\pi \left(\frac{0.15 \times 10^{-3}}{2} \right)^2}$ $(= 27.7 \, \Omega)$	M1
For 7 strands: $\frac{1}{R_{eff}} = 7 \left(\frac{1}{R} \right)$ $R_{eff} = \frac{R}{7}$ $= \frac{(4.9 \times 10^{-7})(1)}{\pi (7) \left(\frac{0.15 \times 10^{-3}}{2} \right)^2}$ $= 3.96 \, \Omega$ $= 4.0 \, \Omega$	A1
5(b)(ii) Potential difference across the $7 \, \Omega$ resistor $= \frac{7}{14+7} \times 12 = 4 \, V$	B1
By potential divider rule, potential difference across $0.9 \, m$ potentiometer $= \frac{0.9 \times 3.96}{3.96+10} \times 12 = 3.06 \, V$	B1
Since the potential difference across the potentiometer is less than the potential difference across the $7 \, \Omega$ resistor, balance length cannot be achieved.	B1