

Question	Marks
6(a) The r.m.s value of an <u>a.c.</u> will give the same <u>heating effect on a resistor</u> as due to <u>a d.c. current</u> of the <u>same value</u> .	B1
6(b)(i) Power = $VI = 1200 \text{ W}$ r.m.s current $I = 1200 / 120 = 10 \text{ A}$ Peak Current $I_o = 10\sqrt{2} = 14.1 \text{ A}$	C1 A1
6(b) (ii) $I = I_o \sin (2\pi f t)$ $= 14.1 \sin (2\pi \times 0.50 t)$ $= 14.1 \sin (100 \pi t)$	B1
6(c) Secondary power = $600 + 1200 = 1800 \text{ W}$ By conservation of energy, Input power = 1800 W $I_p V_p = 1800$ $I_p = 1800 / (2.4 \times 10^3)$ $= 0.75 \text{ A}$	C1 A1

7(a)(i) an electric current that periodically reverses its direction in a circuit (with a B1