

		As indicated from the slope of the V-d graph, $E_X > E_P = E_Y$
	20	A The more the number of parallel connections for the resistors, the lower is the resistance. Short-circuiting any resistance will also reduce the net resistance.
	21	A If only the filament of the fifth bulb has broken, the voltmeter will register a non-zero voltage