

		Short-circuiting any resistance will also reduce the net resistance.
21	A	If only the filament of the fifth bulb has broken, the voltmeter will register a non-zero voltage across the transformer.
22	A	Since B -field is always perpendicular to surface of the iron core it is also always