

As V increases, I increases more than proportional. Thus resistance decreases.

22

Ans: D

For the voltmeter to record zero voltage, the ratio of the resistance $P/Q = R/S$

23

Ans: C