

interference occurs since they occur when for the same amplitude, frequency and speed moving in opposite direction gives rise to stationary wave. {B1}

6 (a)

$$R = \frac{\rho l}{A} = \frac{1.7 \times 10^{-8} \times 1.5}{3.2 \times 10^{-9}} \quad [M1]$$

$$= 8.0 \, \Omega \quad [A0]$$

6 (b)

$$E = IR$$

$$12 = I \times (1.0 + 2.0 + 8.0)$$

$$I = 1.091 \, A \quad [C1]$$

$$I = nAqv$$

$$1.091 = (8.5 \times 10^{28}) (3.2 \times 10^{-9}) (1.6 \times 10^{-19}) v$$

$$v = 0.025 \, m \, s^{-1} \quad [A1]$$

6 (c)(i)

Using potential divider equation,

$$V_{PQ} = \frac{R_{RQ}}{R_{total}} = \frac{8.0}{8.0 + 1.0 + 2.0} \times 12.0 \quad [M1]$$

$$= 8.7 \, V \quad [A0]$$

6 (c)(ii)

$$\text{terminal pd of B} = \frac{R}{R + r} \times E = \frac{4.0}{4.0 + 3.0} \times 1.5$$

$$= 0.857 \, V \quad [C1]$$

$$\frac{V_{PJ}}{V_{PQ}} = \frac{I_{PJ}}{I_{PQ}}$$

Since terminal pd of B = V_{PJ}

$$\frac{0.857}{8.7} = \frac{I_{PJ}}{1.5} \quad [C1]$$

$$I_{PJ} = 0.148 \, A \quad [A1]$$

6 (c)(iii)

To improve accuracy, the modification is either to

1. make the potential difference of PJ larger by increasing the resistance of the $4.0 \, \Omega$ larger [B1].

However this amendment has minimal effect due to the small value of e.m.f. of cell B
Only award 1 mark.

2. make the potential difference per unit length of PQ smaller [M1] to increase the length of PQ needed at balance length by decreasing the e.m.f. of cell A or reducing the resistance of the wire through increasing its cross-sectional area, decreasing length or resistivity or increasing the resistance of the $2.0 \, \Omega$ resistor [A1]

6 (d)

From galvanometer towards J