

		direction of the field lines.
16	C	From Fig. 16.1, when current = 5 mA, p.d. = 0.8 V (across diode) p.d. across 50 Ω resistor = (5 mA)(50 Ω) = 0.25 V Total p.d. across supply = 0.8 + 0.25 = 1.05 V
17	B	Consider circuit B: