

		Total p.d. across supply = $0.8 + 0.25 = \mathbf{1.05\ V}$
17	B	Consider circuit B: By potential divider, p.d across $6\ \text{k}\Omega$ is $\frac{6}{6+2}[8 - (-8)] = 12\ \text{V}$ Potential at J = $8 - 12 = -4\ \text{V}$
18	C	Charge flows = area under the graph