

|      |                                                                                                                                                                                                                                                                                                                                                         |                                       |
|------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------|
|      | Therefore the vertical component of the velocity calculated would be greater.                                                                                                                                                                                                                                                                           |                                       |
|      |                                                                                                                                                                                                                                                                                                                                                         |                                       |
| 6(a) | <p>1.6 J of energy per coulomb means the cell's emf is 1.6 V.</p> <p>This means that the p.d. across the internal resistor is <math>1.6 - 1.2 = 0.4 \text{ V}</math>.</p> <p>Hence the resistance across the internal resistor is</p> <p><math>0.4 / 0.5 = 0.8 \Omega</math> (shown)</p>                                                                | <p>[1] working</p> <p>[1] working</p> |
| (b)  | <p>p.d across the bulb <math>Y = E - Ir</math></p> <p><math>= 1.6 - (0.3)(0.8)</math></p> <p><math>= 1.36 \text{ V}</math></p>                                                                                                                                                                                                                          | <p>[1] sub</p> <p>[1] ans</p>         |
| (c)  | <p>When connected to bulb Y,</p> <p>Total input power <math>= EI = 1.6 \times 0.3 = 0.48 \text{ W}</math></p> <p>Output power <math>= VI = 1.36 \times 0.3 = 0.408 \text{ W}</math></p> <p>Power lost <math>= 0.072 \text{ W}</math></p> <p>Or</p> <p>Power dissipated in internal resistance <math>= I^2 r = (0.3^2)(0.8) = 0.072 \text{ W}</math></p> | <p>[1] working</p> <p>[1] ans</p>     |
| (d)  | <p>Maximum power drawn occurs when <math>R_Z = r</math> (maximum power theorem)</p> <p>Using <math>E = I(R+r)</math></p> <p><math>1.6 = I(0.8+0.8)</math></p> <p><math>I = 1 \text{ A}</math></p>                                                                                                                                                       | <p>[1] working</p> <p>[1] ans</p>     |
|      |                                                                                                                                                                                                                                                                                                                                                         |                                       |
| 7(a) | $eI$                                                                                                                                                                                                                                                                                                                                                    |                                       |