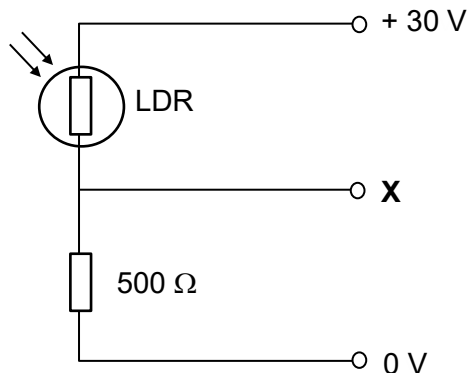


24. The light dependent resistor (LDR) and a  $500\ \Omega$  resistor form a potential divider between voltage lines held at +30 V and 0 V as shown.



The resistance of the LDR is  $1000\ \Omega$  in the dark but drops to  $100\ \Omega$  in bright light.

What is the corresponding change in the potential at **X**?

- A A rise of 25 V
- B A rise of 15 V**
- C A fall of 15 V
- D A fall of 25 V

**Answer: B**

In dark, p.d. across LDR =  $\frac{1000}{1000 + 500} \times 30 = 20\text{ V}$ , so potential at X = +10 V

In bright light, p.d. across LDR =  $\frac{100}{100 + 500} \times 30 = 5\text{ V}$ , so potential at X = +25 V

Change in potential =  $(+25) - (+10) = +15\text{ V}$