

- 20** An electrical source with internal resistance r is used to operate a lamp of resistance R .

What fraction of the total power is delivered to the lamp?

A $\frac{R + r}{R}$

B $\frac{R - r}{R}$

C $\frac{R}{R + r}$

D $\frac{R}{r}$

[Turn over

- 21** A high potential is applied between the electrodes of a hydrogen discharge tube so that the gas