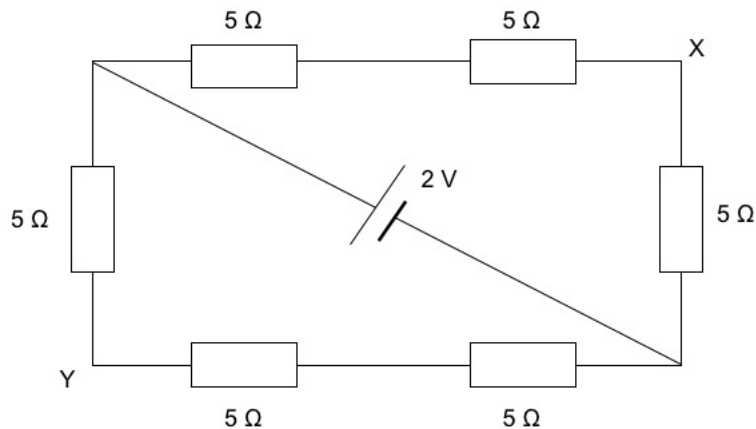


- 22** Six $5\ \Omega$ resistors are connected to a $2\ \text{V}$ cell of negligible internal resistance, as shown in the figure below.



The potential difference between X and Y is

- A** $0\ \text{V}$ **B** $\frac{2}{3}\ \text{V}$ **C** $\frac{8}{9}\ \text{V}$ **D** $\frac{4}{3}\ \text{V}$
- 23** When an alternating power supply of $240\ \text{V r.m.s.}$ is connected across PQ in the circuit shown