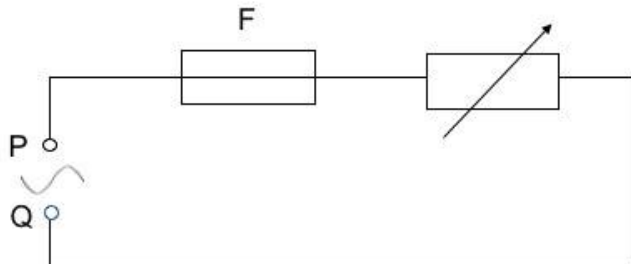


- 23** When an alternating power supply of 240 V r.m.s. is connected across PQ in the circuit shown below.

The fuse F breaks the circuit if the current in it just exceeds 13 A r.m.s.



When the alternating power supply is replaced with a 120 V d.c. source, an identical fuse breaks the circuit if the current just exceeds

A $\frac{13}{2}$ A

B $\frac{13}{\sqrt{2}}$ A

C 13 A

D 26 A

24 An alternating power supply of root-mean-square voltage 4.0 V is connected across a resistive