

23

D

2Ω and 4Ω are connected in series, and they are connected parallel with the cell.

V_{out} is the p.d. across 4Ω

Using potential divider,

$$V_{out} = \frac{4}{4 + 2}(E)$$

$$\frac{V_{out}}{E} = \frac{2}{3}$$

24

D