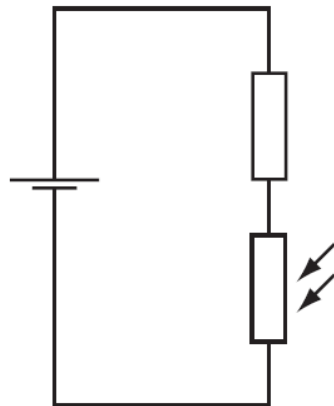
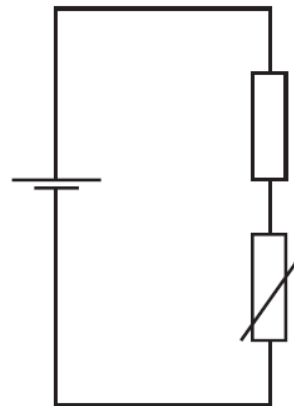


- 23** The diagrams show a NTC light-dependent resistor in circuit P, and a NTC thermistor in circuit Q.



circuit P



circuit Q

How does the potential difference across the fixed resistor in each circuit change when both the brightness of the light on the light-dependent resistor and the temperature of the thermistor are increased?

	circuit P	circuit Q
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases

Answer: D

The resistance across the light-dependent resistor and thermistor will decrease when brightness and temperature increase respectively. By potential divider principle, the potential difference across the light-dependent resistor and thermistor decreases, whereas the potential difference across the fixed resistor increases.