

23 **B** Due to symmetry, **A** and **C** will have the same effective resistance, so they cannot be correct answers.

D has one identical resistor, say R , in parallel with the rest, so the effective resistance will be $< R$.