

24

C

$$\text{Effective resistance of circuit} = \left(\frac{1}{1+1} + \frac{1}{1+5} \right)^{-1} + 1 = 2.5 \text{ k}\Omega$$

$$\text{Current drawn from cell} = 5 / 2.5 = 2.0 \text{ mA}$$

$$\text{Voltmeter reading} = 5 - 2(1) = 3.0 \text{ V}$$

25

C

By conservation of moments