

5 (a)

$$R = \rho \frac{L}{A} = \rho \frac{L}{\left(\pi d^2 / 4\right)} = \frac{4\rho}{\pi} \frac{L}{d^2}$$

M1

$$\frac{R_{AB}}{R_{BC}} = \frac{L_{AB}}{d_{AB}^2} \times \frac{d_{BC}^2}{L_{BC}} \quad \text{OR} \quad \frac{L_{AB}}{L_{BC}} \times \frac{d_{BC}^2}{d_{AB}^2}$$

M1

$$= \frac{50.0}{d^2} \times \frac{(0.3d)^2}{30.0}$$

$$= 0.15$$

A0

(b) From (a)

$$(i) \quad \frac{R_{AB} + R_{BC}}{R_{BC}} = \frac{R_{AB}}{R_{BC}} + 1$$

$$\rightarrow \frac{R_{AC}}{R_{BC}} = \frac{R_{AB}}{R_{BC}} + 1 = 0.15 + 1 = 1.15$$

C1

$$\rightarrow \frac{V_{AC}}{V_{BC}} = 1.15$$

$$V_{AC} = 1.15(2.00) = 2.30 \text{ V}$$

A1

$$(ii) \quad E = V_{AC} + Ir$$

$$2.50 = (2.30) + (0.400)r$$

C1

$$r = 0.500 \, \Omega$$

A1

$$(iii) \quad \text{Efficiency} = \frac{IV_{AC}}{IE} \times 100\%$$

C1

$$= \frac{2.30}{2.50} \times 100\% = 92.0\%$$

A1

- (c) Over-estimate. 0.20 V is actually the p.d. across the internal resistance of cell  $r$  as well as that of the ammeter. **B1**

$$E - V_{AC} = I(r + R_A) \quad \text{B1}$$

$$r + R_A = 0.500 \, \Omega \Rightarrow r < 0.500 \, \Omega$$

- 6 (a) (i) to increase flux linkage (with secondary coil) **B1**