

21 B Current through $L_1 = 60 / 30 = 2.0 \text{ A}$

Current through $L_2 = 45 / 60 = 0.75 \text{ A}$

Current through $R_1 = 2.75$

$R_1 = 60 / 2.75 = 22 \Omega$

22 C Current through $4R = 6.0 \text{ A}$