

- 22 C** Current through $4R = 6.0 \text{ A}$
Current through $4R = 0.5 \times (\text{current through } 2R)$
Current through $2R = 12 \text{ A}$
Total current $= 12 + 6 = 18 \text{ A}$
Total current through R and $3R = 18 \text{ A}$
Current through $R = 3 \times (\text{current through } 3R)$
Current through $3R = 18 / 4 = 4.5 \text{ A}$

- 23 B** The p.d. across LM is less than e.m.f. of the standard cell. Thus, if resistance of LM increased, its