

5a	It is the energy converted per unit charge from electrical to non-electrical when charge is moved through the component.	1 1
5b	Minimum resistance $= \frac{6.0}{6.0} = 1.0 \text{ k}\Omega$ Maximum resistance $= \frac{7.0}{1.2 \times 10^{-3}} = 5.8 \times 10^3 \Omega = 5.8 \text{ k}\Omega$ (Accept a big range of answers for maximum resistance because a one-sided tangent is highly subjective)	1 1 1
5ci	6.0 V	1
5cii	P.d. across $R = 8.0 - 6.0 = 2.0 \text{ V}$ Current through $R = 4.0 + 4.0 = 8.0 \text{ mA}$ Resistance $= \frac{2.0}{8.0 \times 10^{-3}} = 0.25 \times 10^3 \Omega = 0.25 \text{ k}\Omega$	1 1