

			$(1.60 \times 10^{-19}) \times \Delta V = \frac{1}{2} (1.67 \times 10^{-27}) v^2$ $6.03 \times 10^4 \text{ m s}^{-1} < v < 6.64 \times 10^4 \text{ m s}^{-1}$	A1
6	(a)			
		(i)	$V = 5.0 \times 10^{-3} \times 1200 = 6.0 \text{ V}$ $I = 6.0 \div 4700 = 0.00128 \text{ A} \approx 1.3 \text{ mA}$ or 1.28 mA	C1 A1 [2]

		(ii)	resistor: (same pd same resistance hence) no change thermistor: (same pd lower resistance hence) increases B1	[1]
	(b)			
		(i)	Minimum $V_{out} = \frac{2.7}{4.5+2.7} (5.0)$ or Maximum $V_{out} = \frac{2.7}{0.7+2.7} (5.0)$ C1 – An attempt (with substitution) to use the Potential Divider Rule or $V = IR$ Minimum $V_{out} = 1.9$ or 1.88 V A1 Maximum $V_{out} = 4.0$ or 3.97 V A1 (minus 1 mark if wrong min/max)	[3]
		(ii)	(according to the potential divider rule,) potential difference across the resistor very small fraction of 5.0 V or pd across LDR $\approx 5 \text{ V}$ B1 Very low range of V_{out} received or $V_{out} \approx 0$ at all illumination level or very small difference in V_{out} B1 Therefore very low precision of illumination level calculated or high relative (fractional/percentage) uncertainty of illumination level calculated or processing instrument/circuit not sensitive enough to detect small changes in V_{out} B1 (accept V_{out} too small to be detected but max 2 marks, cannot score for 2nd mark)	[3]