

23 C Increasing R_4 increases the effective resistance of the combination of R_2 and R_4 in parallel. By potential divider rule, the p.d. across the parallel combination increases. Since R_2 remains constant, the ammeter reading will increase.

24 D In the driver circuit the p.d. across XY should be minimized so the resistance of the NTC