

remains constant, the ammeter reading will increase.

- 24 D** In the driver circuit, the p.d. across XY should be minimized, so the resistance of the NTC thermistor needs to be maximised, according to potential divider rule. Hence, the temperature should be low.
The terminal p.d. of the test circuit should be maximised, so the resistance of the LDR needs to be maximised. Hence, the environment should be dark.

25 C For coil to remain horizontal