

$$V = 0.01 \text{ m s}$$

7 (a) $f = \frac{1}{T} = \frac{1}{20 \times 10^{-3}} = 50 \text{ Hz}$

(b) $V_{XY,rms} = \frac{17.0}{\sqrt{2}} = 12.0 \text{ V}$

(c) $\frac{N_P}{N_S} = \frac{V_P}{V_S}$
 $\frac{4000}{200} = \frac{V_P}{12.02}$
 $V_P = 240 \text{ V}$

(d) There is a potential difference across the resistor for only half of each cycle.

$$\begin{aligned} \text{mean power} &= \frac{1}{2} \times \frac{V_{rms}^2}{R} \\ &= \frac{1}{2} \times \frac{12.02^2}{4.8} \\ &= 15.1 \text{ W} \end{aligned}$$

(e) For first half of a cycle, from 5 ms to 15 ms, the diode is forward biased and the p.d. across the load resistor is the same as V_{XY} .

5

For the second half of a cycle, from 15 ms to 25 ms, the diode is reverse biased and the p.d. across the load resistor is zero.

9 (2) $T = 4.70 - 1.20 = 3.50 \text{ days}$