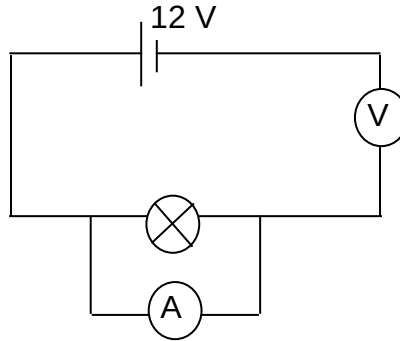


- 19 An ammeter and a voltmeter are connected to a bulb of resistance $4.0\ \Omega$ as shown below.



Which of the following situations is most likely to happen?

- A Ammeter will fuse.
- B Ammeter reads 3.0 A and voltmeter reads 12 V.
- C Ammeter reads zero current and voltmeter reads 12 V.
- D Both ammeter and voltmeter give zero readings.
- C Voltmeter in series, which has very high resistance compared to bulb. The current in the circuit is almost zero, so ammeter reads zero current. The entire emf is across the voltmeter therefore it reads the emf of cell.

- 20 A new rechargeable battery has the marking “500 mA h” printed on it