

$$\frac{E}{R_1 R_2}$$

21 Ans: B

At balance length, current across X is zero, hence terminal p.d. is equal to e.m.f. of X .
Internal resistance therefore does not affect the measurement of e.m.f. of X .

22 Ans: A