

emf and hence induced current in ring. Therefore, ring drops back.

27 Ans: B

When the current from the a.c. sources travels from left to right through the external circuit (during first half cycle), $I = \text{EMF} / \text{total } R = 12 / (4000 + 4000) = 1.5 \text{ mA}$.

When the current from the a.c. sources travels in the other direction (second half cycle), $I = \text{EMF} / \text{total } R = 12 / (6000 + 6000) = 1.0 \text{ mA}$.

Hence, average current through ammeter = $(1.5+1.0)/2 = 1.25 \text{ mA}$

28 Ans: C