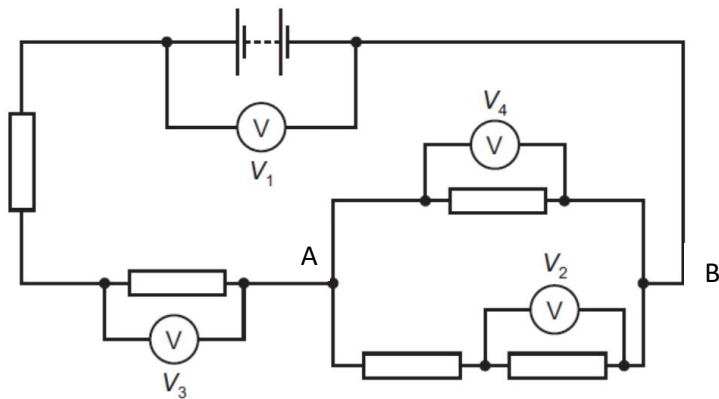


(eg, left to right), and not to be confused with magnetic forces.

- 20 D Ratio of p.d. to current decreases from $\frac{V_0}{I_0}$ to $\frac{V_1}{I_1}$

- 21 B



$$V_4 = 1.0 + 1.0 = 2.0 \text{ V}$$

$$R_{AB} = \frac{2R \times R}{2R + R} = \frac{2}{3}R$$

$$V_3 = \frac{R}{R + R + \frac{2}{3}R} \times 8.0 = 3.0 \text{ V}$$

- 22 A RMS voltage of supply = $12.0/\sqrt{2} = 8.49 \text{ V}$