

	contributes a conventional current of 3 A to the left. Hence the current is 7 A to the left.
20.	Ans: C Since the two wires are in series, the same current will flow through each of them. Hence the ratio is 1.0.
21	Ans: D