

	Hence the ratio is 1.0.
21.	Ans: D Since the diode is reversed biased, as such no current flows in the circuit. Hence the potential difference across the resistors will be zero. Therefore the potential at W and X will be the same (12 V); the potential at Y and Z will be the same (0 V).



