

26.

Ans: B

The five lamps are all parallel to the secondary coil. Current through one lamp = $\frac{24}{12} = 2.0 \text{ A}$

Current through secondary coil, $I_s = 5 \times 2.0 = 10 \text{ A}$

$$V_s I_s = V_p I_p, \quad 12 \times 10 = 240 \times I_p$$
$$I_p = 0.50 \text{ A}$$

27.

Ans: A