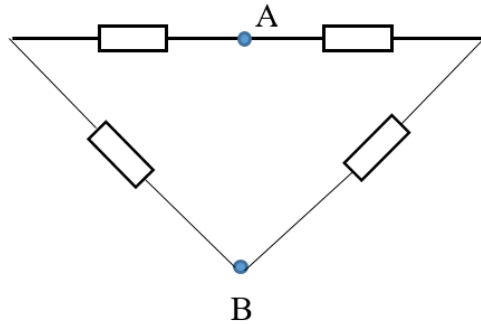


Q16



The two resistors left of A and B are in series with effective resistance $2R$. Similarly the two resistors right of A and B are in series, also with resistance $2R$. The two resistors left of A and B and the two resistors right of A and B are in parallel. Hence

$$\frac{1}{R_{AB}} = \frac{1}{2R} + \frac{1}{2R} = \frac{1}{R}$$

Therefore $R_{AB} = R$

Ans: B

Q17