

24	C	The $2.0\ \Omega$ and $4.0\ \Omega$ resistors are in series. So effective resistance is $6.0\ \Omega$. This $6.0\ \Omega$ resistor is parallel to the given $6.0\ \Omega$, which results in an effective resistance of $3.0\ \Omega$. This $3.0\ \Omega$ resistor is in series with the given $3.0\ \Omega$. Hence, $15\ \text{V}$ is shared equally across both $3.0\ \Omega$ resistors. Hence $7.5\ \text{V}$ appears across the effective resistance of $3.0\ \Omega$ which means $7.5\ \text{V}$ appears across the given $6.0\ \Omega$ resistor.				
25	B				Potential of	