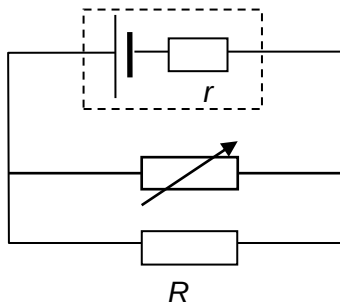


- 19** A battery with an internal resistance r is connected to a variable resistor and a resistor R as shown.

The resistance of the variable resistor is slowly increased from zero to the same value as resistor R .



What happens to the terminal potential difference of the battery?

- A** increases
- B** decreases
- C** decreases before increasing
- D** no change